

Q1 An rms voltage of  $180\text{ V}$  is applied to a device that has a resistance of  $50\Omega$ . Find (a) maximum voltage applied (b) maximum current (c) the rms current supplied.

Q2 An inductor  $L = 0.2\text{ H}$  is connected to a source for which the peak voltage is  $260\text{ V}$  and the frequency is  $50\text{ Hz}$ . What is the peak current?

Q3 A generator is connected across a capacitor of capacitance  $0.65\text{ MF}$ . If the rms voltage and frequency of the generator are  $160\text{ V}$  and  $200\text{ Hz}$  respectively, Find the capacitive reactance and rms current in the circuit.

Q(4): A inductor having a reactance of  $80\ \Omega$  gives off heat at the rate of  $50\ \text{J s}^{-1}$  when it carries a current of  $1.5\ \text{A}$ . Calculate the impedance of the inductor.

Q5: Monochromatic light of wavelength  $689\ \text{nm}$  is used in Young's experiment with two slits separated by a distance of  $1.5 \times 10^{-4}\ \text{m}$ . If the screen is placed at a distance of  $2.5\ \text{m}$  from the slits. Find the distance on the screen between the central fringe and the fourth-order bright fringe.