

PHY121-Applied Physics for Engineers

# Current, Resistance and Ohm's law

LECTURE # 14



By

Muhammad Kaleem Ullah

Lecturer

Department of Physics



## Current and Resistance

**Objectives:** After completing this module, you should be able to:


- Define **electric current** and **electromotive force**.
- Write and apply **Ohm's law** to circuits containing resistance and emf.
- Define **resistivity** of a material and apply formulas for its calculation.
- Define and apply the concept of **temperature coefficient of resistance**.

## Electric Current

**Electric current  $I$**  is the rate of the flow of charge  $Q$  through a cross-section  $A$  in a unit of time  $t$ .

$$I = \frac{Q}{t}$$

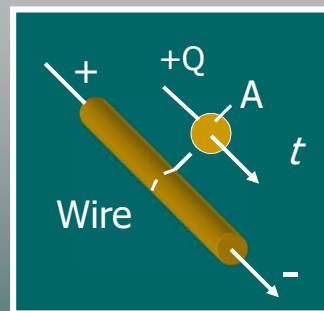
$$1 \text{ A} = \frac{1 \text{ C}}{1 \text{ s}}$$



One ampere A is charge flowing at the rate of one coulomb per second.

**Example 1.** The electric current in a wire is 6 A. How many electrons flow past a given point in a time of 3 s?

$$I = \frac{q}{t}; \quad q = It$$

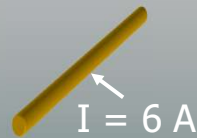

$$q = (6 \text{ A})(3 \text{ s}) = 18 \text{ C}$$


Recall that:  $1 \text{ e}^- = 1.6 \times 10^{-19} \text{ C}$ , then convert:

$$18 \text{ C} = (18 \text{ C}) \left( \frac{1 \text{ e}^-}{1.6 \times 10^{-19} \text{ C}} \right) = 1.125 \times 10^{20} \text{ electrons}$$

In 3 s:  $1.12 \times 10^{20}$  electrons
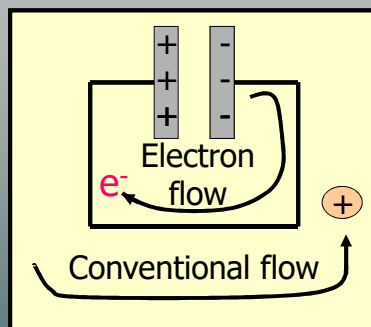
## Conventional Current

Imagine a charged capacitor with  $Q = CV$  that is allowed to discharge.




**Electron flow:** The direction of  $\text{e}^-$  flowing from  $-$  to  $+$ .

**Conventional current:** The motion of  $+q$  from  $+$  to  $-$  has same effect.

Electric fields and potential are defined in terms of  $+q$ , so we will assume conventional current (even if electron flow may be the actual flow).
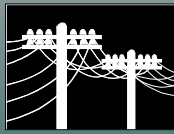
## Electromotive Force


A source of electromotive force (emf) is a device that uses chemical, mechanical or other energy to provide the potential difference necessary for electric current.



Power lines





Battery

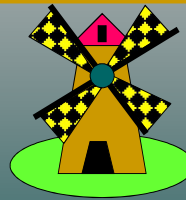

Wind generator

## Water Analogy to EMF

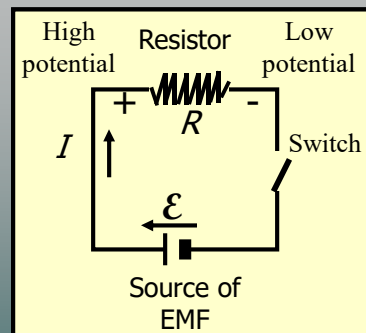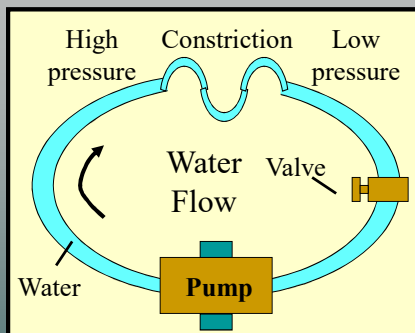


The source of emf (pump) provides the voltage (pressure) to force electrons (water) through electric resistance (narrow constriction).

## Electrical Circuit Symbols


Electrical circuits often contain one or more resistors grouped together and attached to an energy source, such as a battery.

The following symbols are often used:

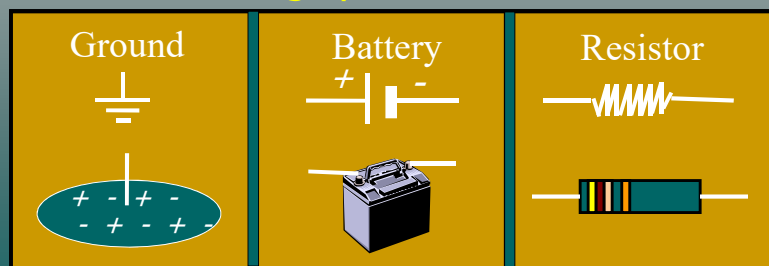
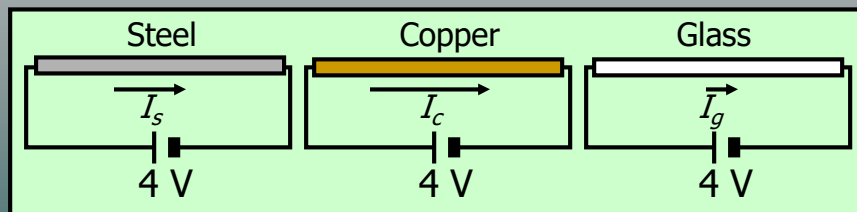
## Electric Resistance

Suppose we apply a constant potential difference of 4 V to the ends of geometrically similar rods of, say: steel, copper, and glass.



The current in glass is much less than for steel or iron, suggesting a property of materials called **electrical resistance  $R$** .

## Ohm's Law

Ohm's law states that the current  $I$  through a given conductor is directly proportional to the potential difference  $V$  between its end points.

$$\text{Ohm's law: } I \propto V$$

Ohm's law allows us to define **resistance**  $R$  and to write the following forms of the law:

$$I = \frac{V}{R}; \quad V = IR; \quad R = \frac{V}{I}$$



Example 2. When a **3-V** battery is connected to a light, a current of **6 mA** is observed. What is the resistance of the light filament?

$$R = \frac{V}{I} = \frac{3.0 \text{ V}}{0.006 \text{ A}}$$


$$R = 500 \, \Omega$$

The **SI unit** for electrical resistance is the **ohm**,  $\Omega$ :
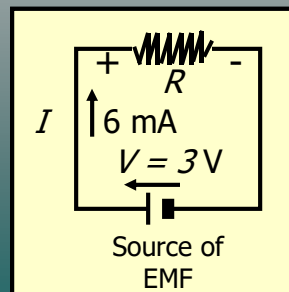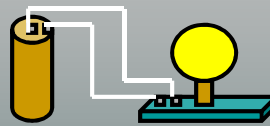
$$1 \, \Omega = \frac{1 \text{ V}}{1 \text{ A}}$$



## Laboratory Circuit Symbols

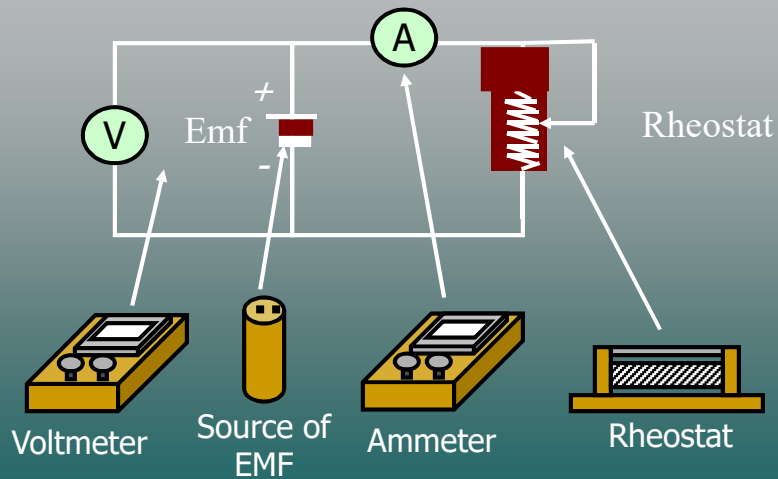

## Factors Affecting Resistance

1. The **length L** of the material. Longer materials have greater resistance.



2. The cross-sectional **area A** of the material. Larger areas offer **LESS** resistance.



## Factors Affecting R (Cont.)

3. The **temperature**  $T$  of the material. The higher temperatures usually result in **higher** resistances.



4. The kind of **material**. Iron has more electrical resistance than a geometrically similar copper conductor.



## Resistivity of a Material

The *resistivity*  $\rho$  is a property of a material that determines its electrical resistance  $R$ .

Recalling that  $R$  is directly proportional to length  $L$  and inversely proportional to area  $A$ , we may write:

$$R = \rho \frac{L}{A} \quad \text{or} \quad \rho = \frac{RA}{L}$$

The unit of resistivity is the **ohm-meter** ( $\Omega \cdot \text{m}$ )



**Example 3.** What **length  $L$**  of copper wire is required to produce a  **$4 \text{ m}\Omega$**  resistor? Assume the diameter of the wire is  **$1 \text{ mm}$**  and that the resistivity  **$\rho$**  of copper is  **$1.72 \times 10^{-8} \Omega\cdot\text{m}$** .

$$A = \frac{\pi D^2}{4} = \frac{\pi (0.001 \text{ m})^2}{4} \quad A = 7.85 \times 10^{-7} \text{ m}^2$$

$$R = \rho \frac{L}{A} \quad L = \frac{RA}{\rho} = \frac{(0.004 \Omega)(7.85 \times 10^{-7} \text{ m}^2)}{1.72 \times 10^{-8} \Omega\cdot\text{m}}$$

Required length is:

$$L = 0.183 \text{ m}$$

## Temperature Coefficient

For most materials, the resistance  **$R$**  changes in proportion to the initial resistance  **$R_0$**  and to the change in temperature  **$\Delta t$** .

**Change in  
resistance:**

$$\Delta R = \alpha R_0 \Delta t$$

The temperature coefficient of resistance,  **$\alpha$**  is the change in resistance per unit resistance per unit degree change of temperature.

$$\alpha = \frac{\Delta R}{R_0 \Delta t}; \quad \text{Units: } \frac{1}{^\circ\text{C}}$$

Example 4. The resistance of a copper wire is  $4.00 \text{ m}\Omega$  at  $20^\circ\text{C}$ . What will be its resistance if heated to  $80^\circ\text{C}$ ? Assume that  $\alpha = 0.004 / ^\circ\text{C}$ .

$$R_0 = 4.00 \text{ m}\Omega; \quad \Delta t = 80^\circ\text{C} - 20^\circ\text{C} = 60^\circ\text{C}$$

$$\Delta R = \alpha R_0 \Delta t; \quad \Delta R = (0.004 / ^\circ\text{C})(4 \text{ m}\Omega)(60^\circ\text{C})$$

$$\Delta R = 1.03 \text{ m}\Omega \quad R = R_0 + \Delta R$$

$$R = 4.00 \text{ m}\Omega + 1.03 \text{ m}\Omega$$

$$R = 5.03 \text{ m}\Omega$$

## Electric Power


Electric power  $P$  is the rate at which electric energy is expended, or work per unit of time.

To charge  $C$ : Work =  $qV$

$$P = \frac{\text{Work}}{t} = \frac{qV}{t} \quad \text{and} \quad I = \frac{q}{t}$$

Substitute  $q = It$ , then:
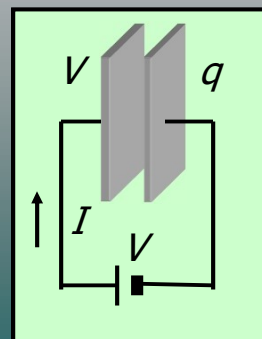
$$P = \frac{VI\cancel{t}}{\cancel{t}} \quad \Rightarrow \quad P = VI$$



## Calculating Power

Using Ohm's law, we can find electric **power** from any two of the following parameters: **current**  $I$ , **voltage**  $V$ , and **resistance**  $R$ .

Ohm's law:  $V = IR$

$$P = VI; \quad P = I^2 R; \quad P = \frac{V^2}{R}$$

**Example 5.** A power tool is rated at **9 A** when used with a circuit that provides **120-V**. What power is used in operating this tool?

$$P = VI = (120 \text{ V})(9 \text{ A})$$

$$P = 1080 \text{ W}$$

**Example 6.** A 500-W heater draws a current of 10 A. What is the resistance?

$$P = I^2 R; \quad R = \frac{P}{I^2} = \frac{500 \text{ W}}{(10 \text{ A})^2}$$

$$R = 5.00 \, \Omega$$

## Summary of Formulas

Electric  
current:

$$I = \frac{Q}{t}$$

$$1 \text{ A} = \frac{1 \text{ C}}{1 \text{ s}}$$

Ohm's Law

$$I = \frac{V}{R}; \quad V = IR; \quad R = \frac{V}{I}$$

$$\text{Resistance: } 1 \text{ ohm} = \frac{1 \text{ volt}}{1 \text{ ampere}}$$

## Summary (Cont.)

Resistivity of  
materials:

$$R = \rho \frac{L}{A} \quad \text{or} \quad \rho = \frac{RA}{L}$$

Temperature coefficient of resistance:

$$\Delta R = \alpha R_0 \Delta t$$

$$\alpha = \frac{\Delta R}{R_0 \Delta t}; \quad \text{Units: } \frac{1}{\text{C}^0}$$

Electric  
Power  $P$ :

$$P = VI; \quad P = I^2 R; \quad P = \frac{V^2}{R}$$

## CONCLUSION: Chapter 27 Current and Resistance

