



COMSATS University Islamabad (CUI), Lahore Campus
Department of Electrical & Computer Engineering

Lab Assignment 3

Name: _____

Registration No: _____

Class: SP23-BCS-A
Subject: Digital Logic Design
Instructor: Sarmad Hassan

Marks: 10
Due Date: 07-12-2023

INSTRUCTIONS

- Do all the necessary workings and attach it with exam sheet.
- Add the screenshot of complete window, half/cropped screenshot is not acceptable.
- Copied assignments will be marked as zero.

Question: 1

- A. Differentiate between different types of shift registers.
- B. Implement all types of shift registers proteus using input as 1101 and verify the outputs.