



COMSATS University Islamabad (CUI), Lahore Campus
Department of Electrical & Computer Engineering

Lab Assignment

Name: _____

Registration No: _____

Class: SP23-BCS-A
Subject: Digital Logic Design
Instructor: Sarmad Hassan

Marks: 10
Due Date: 12-10-2023

INSTRUCTIONS

- Do all the necessary workings and attach it with answer sheet.
- No marks will be given without complete working and complete simulation window screenshot.
- Add the screenshot of complete window, half/cropped screenshot is not acceptable.
- Copied assignments will be marked as zero.

Question: 1

A. Design a logic circuit having 3 inputs, A, B, C will have its output HIGH only when a majority of the inputs are HIGH.

B. Design a logic circuit based on the criteria given below:

Car alarm will sound when car Alarm is activated **and** either Car is shaken or car lock open with key or someone tries to start the car when doors are locked

Use the following notations:

A= Alarm Activated

B= Car Shake

C = lock Open with key

D= Car starts when doors are locked.

C. Implement the designed circuit in part A and B on proteus to verify the outputs.