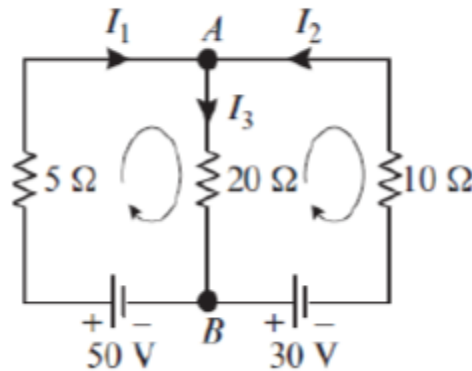


## Solution Quiz No 1: Class SP22-BCS-A & C

**Q1:** Determine currents  $I_1$ ,  $I_2$  and  $I_3$  in the circuit below using Gauss-Elimination method.



**Solution** Using the assigned directions for the currents, Kirchhoff's current law provides one equation for each node:

Node	Current In		Current Out
A	$I_1 + I_2$	=	$I_3$
B	$I_3$	=	$I_1 + I_2$

	Voltage Rises	Voltage Drops
<b>Left Inside Loop</b>	50	$5I_1 + 20I_3$
<b>Right Inside Loop</b>	$30 + 10I_2 + 20I_3$	0
<b>Outside Loop</b>	$30 + 50 + 10I_2$	$5I_1$

These conditions can be rewritten as

$$\begin{aligned}
 5I_1 + 20I_3 &= 50 \\
 10I_2 + 20I_3 &= -30 \\
 5I_1 - 10I_2 &= 80
 \end{aligned}$$

Now mathematical model of above circuit is

$$I_1 + I_2 - I_3 = 0$$

$$5I_1 + 20I_3 = 50$$

$$10I_2 + 20I_3 = -30$$

$$5I_1 - 10I_2 = 80$$

$$[A|b] = \left[ \begin{array}{ccc|c} 1 & 1 & -1 & 0 \\ 5 & 0 & 20 & 50 \\ 0 & 10 & 20 & -30 \\ 5 & -10 & 0 & 80 \end{array} \right]$$

Apply row operations yourself (*I am using linear algebra toolkit*)

$$\sim \left[ \begin{array}{ccc|c} 1 & 0 & 0 & 6 \\ 0 & 1 & 0 & -5 \\ 0 & 0 & 1 & 1 \\ 0 & 0 & 0 & 0 \end{array} \right]$$

$$I_1 = 6; \quad I_2 = -5; \quad I_3 = 1$$

**Question 2:** Write matrices  $A$  and  $A^{-1}$  as a product of elementary matrices.

$$A = \begin{bmatrix} 1 & -1 & 3 \\ 0 & 1 & -1 \\ 1 & 0 & 3 \end{bmatrix}$$

**Solution:-**

$$[A|I] = \left[ \begin{array}{ccc|ccc} 1 & -1 & 3 & 1 & 0 & 0 \\ 0 & 1 & -1 & 0 & 1 & 0 \\ 1 & 0 & 3 & 0 & 0 & 1 \end{array} \right] \sim \left[ \begin{array}{ccc|ccc} 1 & -1 & 3 & 1 & 0 & 0 \\ 0 & 1 & -1 & 0 & 1 & 0 \\ 0 & 1 & 0 & -1 & 0 & 1 \end{array} \right] R_3 - R_1$$

$$R \sim \left[ \begin{array}{ccc|ccc} 1 & -1 & 3 & 1 & 0 & 0 \\ 0 & 1 & -1 & 0 & 1 & 0 \\ 0 & 0 & 1 & -1 & -1 & 1 \end{array} \right] R_3 - R_2 \sim \left[ \begin{array}{ccc|ccc} 1 & 0 & 2 & 1 & 1 & 0 \\ 0 & 1 & -1 & 0 & 1 & 0 \\ 0 & 0 & 1 & -1 & -1 & 1 \end{array} \right] R_1 + R_2$$

$$\sim \left[ \begin{array}{ccc|ccc} 1 & 0 & 0 & 3 & 3 & -2 \\ 0 & 1 & 0 & 0 & 1 & 1 \\ 0 & 0 & 1 & -1 & -1 & 1 \end{array} \right] \begin{array}{l} R_1 - 2R_3 \\ R_2 + R_3 \end{array}$$

We Know  $A^{-1} = E_5 E_4 E_3 E_2 E_1$  and  $A = E_1^{-1} E_2^{-1} E_3^{-1} E_4^{-1} E_5^{-1}$

$$E_1 = \left[ \begin{array}{ccc} 1 & 0 & 0 \\ 0 & 1 & 0 \\ -1 & 0 & 1 \end{array} \right] R_3 - R_1 \text{ and } E_1^{-1} = \left[ \begin{array}{ccc} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 1 & 0 & 1 \end{array} \right]$$

$$E_2 = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix} R_3 - R_2 \text{ and } E_2^{-1} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 1 & 1 \end{bmatrix}$$

$$E_3 = \begin{bmatrix} 1 & 1 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} R_1 + R_2 \text{ and } E_3^{-1} = \begin{bmatrix} 1 & -1 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

$$E_4 = \begin{bmatrix} 1 & 0 & -2 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} R_1 - 2R_3 \text{ and } E_4^{-1} = \begin{bmatrix} 1 & 0 & 2 \\ 0 & 1 & 0 \\ 1 & 0 & 1 \end{bmatrix}$$

$$E_5 = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 1 \\ 0 & 0 & 1 \end{bmatrix} R_2 + R_3 \text{ and } E_5^{-1} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & -1 \\ 1 & 0 & 1 \end{bmatrix}$$